
CONTENTS

Chapter 1 Power Electronics and Drives: Enabling Technologies

- 1-1 Introduction to Power Electronics and Drives
- 1-2 Applications and the Role of Power Electronics and Drives
- 1-3 Energy and the Environment
- 1-4 Need for High Efficiency and High Power Density
- 1-5 Structure of Power Electronics Interface
- 1-6 The Switch-Mode Load-Side Converter
- 1-7 Recent and Potential Advancements
- References
- Problems

Chapter 2 Design of Switching Power-Pole

- 2-1 Power Transistors and Power Diodes
- 2-2 Selection of Power Transistors
- 2-3 Selection of Power Diodes
- 2-4 Switching Characteristics and Power Losses in Power-Poles
- 2-5 Justifying Switches and Diodes as Ideal
- 2-6 Design Considerations
- 2-7 The PWM Controller IC
- References
- Problems

Chapter 3 Switch-Mode DC-DC Converters: Switching Analysis, Topology Selection and Design

- 3-1 DC-DC Converters
- 3-2 Switching Power-Pole in DC Steady State
- 3-3 Simplifying Assumptions
- 3-4 Common Operating Principles
- 3-5 Buck Converter Switching Analysis in DC Steady State

- 3-6 Boost Converter Switching Analysis in DC Steady State
- 3-7 Buck-Boost Converter Switching Analysis in DC Steady State
- 3-8 Topology Selection
- 3-9 Worst-Case Design
- 3-10 Synchronous-Rectified Buck Converter for Very Low Output Voltages
- 3-11 Interleaving of Converters
- 3-12 Regulation of DC-DC Converters by PWM
- 3-13 Dynamic Average Representation of Converters in CCM
- 3-14 Bi-Directional Switching Power-Pole
- 3-15 Discontinuous-Conduction Mode (DCM)
- References
- Problems

Appendix 3A Discontinuous-Conduction Mode (DCM) in DC-DC Converters

Chapter 4 Designing Feedback Controllers in Switch-Mode DC Power Supplies

- 4-1 Objectives of Feedback Control
- 4-2 Review of the Linear Control Theory
- 4-3 Linearization of Various Transfer Function Blocks
- 4-4 Feedback Controller Design in Voltage-Mode Control
- 4-5 Peak-Current Mode Control
- 4-6 Feedback Controller Design in DCM
- References
- Problems

Chapter 5 Rectification of Utility Input Using Diode Rectifiers

- 5-1 Introduction
- 5-2 Distortion and Power Factor
- 5-3 Classifying the “Front-End” of Power Electronic Systems
- 5-4 Diode-Rectifier Bridge “Front-Ends”
- 5-5 Means to Avoid Transient Inrush Currents at Starting
- 5-6 Front-Ends with Bi-Directional Power Flow
- References
- Problems

Chapter 6 Power-Factor-Correction (PFC) Circuits and Designing the Feedback Controller

- 6-1 Introduction
- 6-2 Single-Phase PFCs
- 6-3 Control of PFCs
- 6-4 Designing the Inner Average-Current-Control Loop
- 6-5 Designing the Outer Voltage Loop
- 6-6 Example of Single-Phase PFC Systems
- 6-7 Simulation Results
- 6-8 Feedforward of the Input Voltage
- References
- Problems

Chapter 7 Magnetic Circuit Concepts

- 7-1 Ampere-Turns and Flux
- 7-2 Inductance L
- 7-3 Faraday's Law: Induced Voltage in a Coil due to Time-Rate of Change of Flux Linkage
- 7-4 Leakage and Magnetizing Inductances
- 7-5 Transformers
- References
- Problems

Chapter 8 Switch-Mode DC Power Supplies

- 8-1 Applications of Switch-Mode DC Power Supplies
- 8-2 Need for Electrical Isolation
- 8-3 Classification of Transformer-Isolated DC-DC Converters
- 8-4 Flyback Converters
- 8-5 Forward Converters
- 8-6 Full-Bridge Converters
- 8-7 Half-Bridge and Push-Pull Converters
- 8-8 Practical Considerations
- References
- Problems

Chapter 9 Design of High-Frequency Inductors and Transformers

- 9-1 Introduction
- 9-2 Basics of Magnetic Design

- 9-3 Inductor and Transformer Construction
- 9-4 Area-Product Method
- 9-5 Design Example of an Inductor
- 9-6 Design Example of a Transformer for a Forward Converter
- 9-7 Thermal Considerations
- References
- Problems

Chapter 10 Soft-Switching In DC-DC Converters And Inverters For Induction Heating And Compact Fluorescent Lamps

- 10-1 Introduction
- 10-2 Hard-Switching In the Switching Power-Poles
- 10-3 Soft-Switching In the Switching Power-Poles
- 10-4 Inverters for Induction Heating and Compact Fluorescent Lamps
- References
- Problems

Chapter 11 Electric Motor Drives

- 11-1 Introduction
- 11-2 Mechanical System Requirements
- 11-3 Introduction to Electric Machines and the Basic Principles of Operation
- 11-4 DC Motors
- 11-5 Permanent-Magnet AC Machines
- 11-6 Induction Machines
- 11-7 Summary
- References
- Problems

Chapter 12 Synthesis of DC and Low-Frequency Sinusoidal AC Voltages for Motor Drives and UPS

- 12-1 Introduction
- 12-2 Switching Power-Pole as the Building Block
- 12-3 DC-Motor Drives
- 12-4 AC-Motor Drives
- 12-5 Voltage-Link Structure with Bi-Directional Power Flow
- 12-6 Uninterruptible Power Supplies (UPS)
- References
- Problems

Chapter 13 Designing Feedback Controllers for Motor Drives

- 13-1 Introduction
- 13-2 Control Objectives
- 13-3 Cascade Control Structure
- 13-4 Steps in Designing the Feedback Controller
- 13-5 System Representation for Small-Signal Analysis
- 13-6 Controller Design
- 13-7 Example of a Controller Design
- References
- Problems

Chapter 14 Thyristor Converters

- 14-1 Introduction
- 14-2 Thyristors (SCRs)
- 14-3 Single-Phase, Phase-Controlled Thyristor Converters
- 14-4 Three-Phase, Full-Bridge Thyristor Converters
- 14-5 Current-Link Systems
- References
- Problems

Chapter 15 Utility Applications of Power Electronics

- 15-1 Introduction
- 15-2 Power Semiconductor Devices and Their Capabilities
- 15-3 Categorizing Power Electronic Systems
- 15-4 Distributed Generation (DG) Applications
- 15-5 Power Electronic Loads
- 15-6 Power Quality Solutions
- 15-7 Transmission and Distribution (T&D) Applications
- References
- Problems