
Contents

Series Introduction H. Lee Willis
Preface

1 Basic Transformer Theory

- 1.1 Definition of a Transformer
- 1.2 Magnetic Units and Conversion Factors
- 1.3 Currents and Magnetic Fields
- 1.4 Magnetic Induction
- 1.5 Constructing a Simple Transformer
- 1.6 The Magnetic Circuit
- 1.7 The B - H Curve
- 1.8 The B - H Curve and Hysteresis
- 1.9 Magnetizing Currents and Harmonics
- 1.10 Transformer Core Design and Construction
- 1.11 Magnetostriction
- 1.12 Completing the Transformer by Adding a Second Winding

- 1.13 Placement of the Windings
- References

2 Two-Winding Transformer Connections

- 2.1 Introduction
- 2.2 The Y-Y Connection in Three-Phase Systems
- 2.3 Advantages of the Y-Y Connection
- 2.4 Disadvantages of the Y-Y Connection
- 2.5 The Y- Δ Connection and the Δ -Y Connection
- 2.6 Phase Angle Displacement and Phase Rotation
- 2.7 The Y- Δ Grounding Bank
- 2.8 The Zigzag Connection
- 2.9 Comparisons of Economy of the Different Winding Configurations
- 2.10 Trade-Off Between Steel and Copper in the Design of a Transformer
- 2.11 Connecting Three-Phase Banks Using Single-Phase Transformers
- 2.12 Transforming Three-Phase Voltages into Two-Phase Voltages
- 2.13 The Scott Transformer Connection
- 2.14 Three-Phase Transformer Designs
- 2.15 Standard Terminal Markings for Transformers
- References

3 Transformer Impedance and Losses

- 3.1 Leakage Flux and Leakage Reactance
- 3.2 Conductor Losses
- 3.3 No-Load Losses
- 3.4 Magnetizing Reactance
- 3.5 Equivalent Circuit of a Two-Winding Transformer
- 3.6 A Brief Tutorial on Symmetrical Components
- 3.7 Transformer Equivalent Circuits Modeled in Zero Phase Sequence Networks
- 3.8 Series Impedance and Regulation
- 3.9 Matching Transformers for Parallel and Bank Operations

- 3.10 Impedance Mismatch in Three-Phase Transformer Banks
 - 3.11 Temperature Rise and the Thermal Capability
 - 3.12 Interpreting Transformer Test Reports
 - 3.13 Calculating the Hot-Spot Temperature Using the IEEE Method
 - 3.14 Calculating the Loss of Life
- References

4 Autotransformers and Three-Winding Transformers

- 4.1 Autotransformer Connections
 - 4.2 Impedance of an Autotransformer
 - 4.3 Limitations of the Autotransformer Connection
 - 4.4 Autotransformer Voltages with Short Circuits Applied
 - 4.5 Impulse Voltages Applied to Autotransformers
 - 4.6 Autotransformer Core and Coil Designs and Terminal Configurations
 - 4.7 Advantages and Disadvantages of the Autotransformer Connection
 - 4.8 Three-Winding Transformers
 - 4.9 Modification of Transformer Laws with Three Windings
 - 4.10 Equivalent Circuit of a Three-Winding Transformer
 - 4.11 Core and Coil Construction of Three-Winding Transformers
 - 4.12 Thermal Capability of Three-Winding Transformers
 - 4.13 The Stabilizing Effect of a Δ Tertiary Winding
- Reference

5 Short Circuits, Inrush Currents, and Other Phenomena

- 5.1 Effects of Short Circuits on Transformers
- 5.2 Comparisons of Short-Circuit Currents for Various Faults
- 5.3 Mechanical Forces in Transformers
- 5.4 Forces between Transformer Windings
- 5.5 Short-Circuit Forces in Three-Winding Transformers
- 5.6 Exciting Current Inrush
- 5.7 Tank Overheating from Zero-Sequence Currents

Contents

Series Introduction H. Lee Willis
Preface

1 Basic Transformer Theory

- 1.1 Definition of a Transformer
- 1.2 Magnetic Units and Conversion Factors
- 1.3 Currents and Magnetic Fields
- 1.4 Magnetic Induction
- 1.5 Constructing a Simple Transformer
- 1.6 The Magnetic Circuit
- 1.7 The B - H Curve
- 1.8 The B - H Curve and Hysteresis
- 1.9 Magnetizing Currents and Harmonics
- 1.10 Transformer Core Design and Construction
- 1.11 Magnetostriction
- 1.12 Completing the Transformer by Adding a Second Winding

- 1.13 Placement of the Windings
- References

2 Two-Winding Transformer Connections

- 2.1 Introduction
- 2.2 The Y-Y Connection in Three-Phase Systems
- 2.3 Advantages of the Y-Y Connection
- 2.4 Disadvantages of the Y-Y Connection
- 2.5 The Y- Δ Connection and the Δ -Y Connection
- 2.6 Phase Angle Displacement and Phase Rotation
- 2.7 The Y- Δ Grounding Bank
- 2.8 The Zigzag Connection
- 2.9 Comparisons of Economy of the Different Winding Configurations
- 2.10 Trade-Off Between Steel and Copper in the Design of a Transformer
- 2.11 Connecting Three-Phase Banks Using Single-Phase Transformers
- 2.12 Transforming Three-Phase Voltages into Two-Phase Voltages
- 2.13 The Scott Transformer Connection
- 2.14 Three-Phase Transformer Designs
- 2.15 Standard Terminal Markings for Transformers
- References

3 Transformer Impedance and Losses

- 3.1 Leakage Flux and Leakage Reactance
- 3.2 Conductor Losses
- 3.3 No-Load Losses
- 3.4 Magnetizing Reactance
- 3.5 Equivalent Circuit of a Two-Winding Transformer
- 3.6 A Brief Tutorial on Symmetrical Components
- 3.7 Transformer Equivalent Circuits Modeled in Zero Phase Sequence Networks
- 3.8 Series Impedance and Regulation
- 3.9 Matching Transformers for Parallel and Bank Operations

- 3.10 Impedance Mismatch in Three-Phase Transformer Banks
 - 3.11 Temperature Rise and the Thermal Capability
 - 3.12 Interpreting Transformer Test Reports
 - 3.13 Calculating the Hot-Spot Temperature Using the IEEE Method
 - 3.14 Calculating the Loss of Life
- References

4 Autotransformers and Three-Winding Transformers

- 4.1 Autotransformer Connections
 - 4.2 Impedance of an Autotransformer
 - 4.3 Limitations of the Autotransformer Connection
 - 4.4 Autotransformer Voltages with Short Circuits Applied
 - 4.5 Impulse Voltages Applied to Autotransformers
 - 4.6 Autotransformer Core and Coil Designs and Terminal Configurations
 - 4.7 Advantages and Disadvantages of the Autotransformer Connection
 - 4.8 Three-Winding Transformers
 - 4.9 Modification of Transformer Laws with Three Windings
 - 4.10 Equivalent Circuit of a Three-Winding Transformer
 - 4.11 Core and Coil Construction of Three-Winding Transformers
 - 4.12 Thermal Capability of Three-Winding Transformers
 - 4.13 The Stabilizing Effect of a Δ Tertiary Winding
- Reference

5 Short Circuits, Inrush Currents, and Other Phenomena

- 5.1 Effects of Short Circuits on Transformers
- 5.2 Comparisons of Short-Circuit Currents for Various Faults
- 5.3 Mechanical Forces in Transformers
- 5.4 Forces between Transformer Windings
- 5.5 Short-Circuit Forces in Three-Winding Transformers
- 5.6 Exciting Current Inrush
- 5.7 Tank Overheating from Zero-Sequence Currents

- 5.8 Primary Fuse Misoperations
- 5.9 Ferroresonance
- 5.10 Voltage Surges
- References

6 Ancillary Equipment

- 6.1 Bushings
- 6.2 Oil Preservation Systems
- 6.3 Cooling Equipment
- 6.4 Temperature, Oil Level, and Pressure Gauges
- 6.5 Tap-Changing Equipment
- 6.6 Load Tap Changers
- 6.7 Voltage Regulating Transformers
- 6.8 Tap Changer Automatic Controls
- 6.9 Variable Phase Shifting Transformers
- Reference

7 Reading and Applying Nameplate Information

- 7.1 Minimum Nameplate Requirements
- 7.2 Manufacturer's Information
- 7.3 Cooling Class, Number of Phases, and Operating Frequency
- 7.4 Voltage Ratings
- 7.5 KVA or MVA Ratings
- 7.6 Winding Connection Diagram
- 7.7 Phasor or Vector Diagram
- 7.8 Weights and Oil Capacity
- 7.9 Operating Pressure Range
- 7.10 Impedance
- 7.11 Basic Insulation Level
- 7.12 Nameplate Layout
- References

8 Maintenance, Testing, Troubleshooting, and Reliability

- 8.1 Good Utility Practices
- 8.2 Preventative Maintenance versus Predictive Maintenance

- 8.3 Factory Tests
- 8.4 Ratio Test
- 8.5 Other Factory Tests
- 8.6 Field Tests
- 8.7 Gas-in-Oil Analysis
- 8.8 Water-in-Oil Analysis
- 8.9 Drying Transformers
- 8.10 Oil Dielectric Test
- 8.11 Reliability Calculations
- 8.12 The Chi-Squared Distribution
- 8.13 The Poisson Distribution
- 8.14 Statistical Economics
- References